



Ch9 (补充内容) Memory and FPGA



Main contents:

1、Memory types

☀ Read Only Memory (ROM)

Mask ROM、 PROM、 EPROM、 EEPROM、 FLASH

☀ Random Access Memory (RAM)

Static SRAM、 Dynamic DRAM

☀ Sequential Access Memory (SAM)

FIFO、 FILO

2、 Basic functions and internal structure of ROMs

3、 Using ROMs for Combinational Logic

4、 SRAM and the expanding of RAM



Types Of ROMs

☀ Mask ROM

- ☀ Connections made by the semiconductor vendor
- ☀ Expensive setup cost, Several weeks for delivery. High volume only
- ☀ Bipolar or MOS technology

☀ PROM

- ☀ Programmable ROM
- ☀ Vaporize (blow) fusible links with PROM programmer using high voltage/current pulses
- ☀ Bipolar technology
- ☀ One-time programmable

☀ EPROM

- ☀ Erasable Programmable ROM
- ☀ Charge trapped on extra “floating gate” of MOS transistors
- ☀ Exposure to UV light removes charge. Limited number of erasures (10-100)



☀ **EEPROM (E²ROM)**

- ☀ **Electrically Erasable ROM**
- ☀ **Not RAM (relatively slow charge/discharge)**
- ☀ **limited number of charge/discharge cycles (10,000)**



☀ **Flash**

- ☀ **Electronically erasable in blocks**
- ☀ **100,000 erase cycles**
- ☀ **Simpler and denser than EEPROM**



Basic functions of ROMs

  - ★ A combinational circuit with n inputs and b outputs:




00	0101
01	1011
10	0100
11	1110

address		data			
A_1	A_0	D_3	D_2	D_1	D_0
0	0	0	1	0	1
0	1	1	0	1	1
1	0	0	1	0	0
1	1	1	1	1	0



A 4x4 multiplier using a 256x8 ROM

 

Use a C-program to generate this table


Hexadecimal Text File Specifying the Contents of a 4 × 4 Multiplier ROM

```
00: 00 00 00 00 00 00 00 00 00 00 00 00 00 00 00 00
10: 00 01 02 03 04 05 06 07 08 09 0A 0B 0C 0D 0E 0F
20: 00 02 04 06 08 0A 0C 0E 10 12 14 16 18 1A 1C 1E
30: 00 03 06 09 0C 0F 12 15 18 1B 1E 21 24 27 2A 2D
40: 00 04 08 0C 10 14 18 1C 20 24 28 2C 30 34 38 3C
50: 00 05 0A 0F 14 19 1E 23 28 2D 32 37 3C 41 46 4B
60: 00 06 0C 12 18 1E 24 2A 30 36 3C 42 48 4E 54 5A
70: 00 07 0E 15 1C 23 2A 31 38 3F 46 4D 54 5B 62 69
80: 00 08 10 18 20 28 30 38 40 48 50 58 60 68 70 78
90: 00 09 12 1B 24 2D 36 3F 48 51 5A 63 6C 75 7E 87
A0: 00 0A 14 1E 28 32 3C 46 50 5A 64 6E 78 82 8C 96
B0: 00 0B 16 21 2C 37 42 4D 58 63 6E 79 84 8F 9A A5
C0: 00 0C 18 24 30 3C 48 54 60 6C 78 84 90 9C A8 B4
D0: 00 0D 1A 27 34 41 4E 5B 68 75 82 8F 9C A9 B6 C3
E0: 00 0E 1C 2A 38 46 54 62 70 7E 8C 9A A8 B6 C4 D2
F0: 00 0F 1E 2D 3C 4B 5A 69 78 87 96 A5 B4 C3 D2 E1
```



Logic diagram of a 8x4 diode ROM

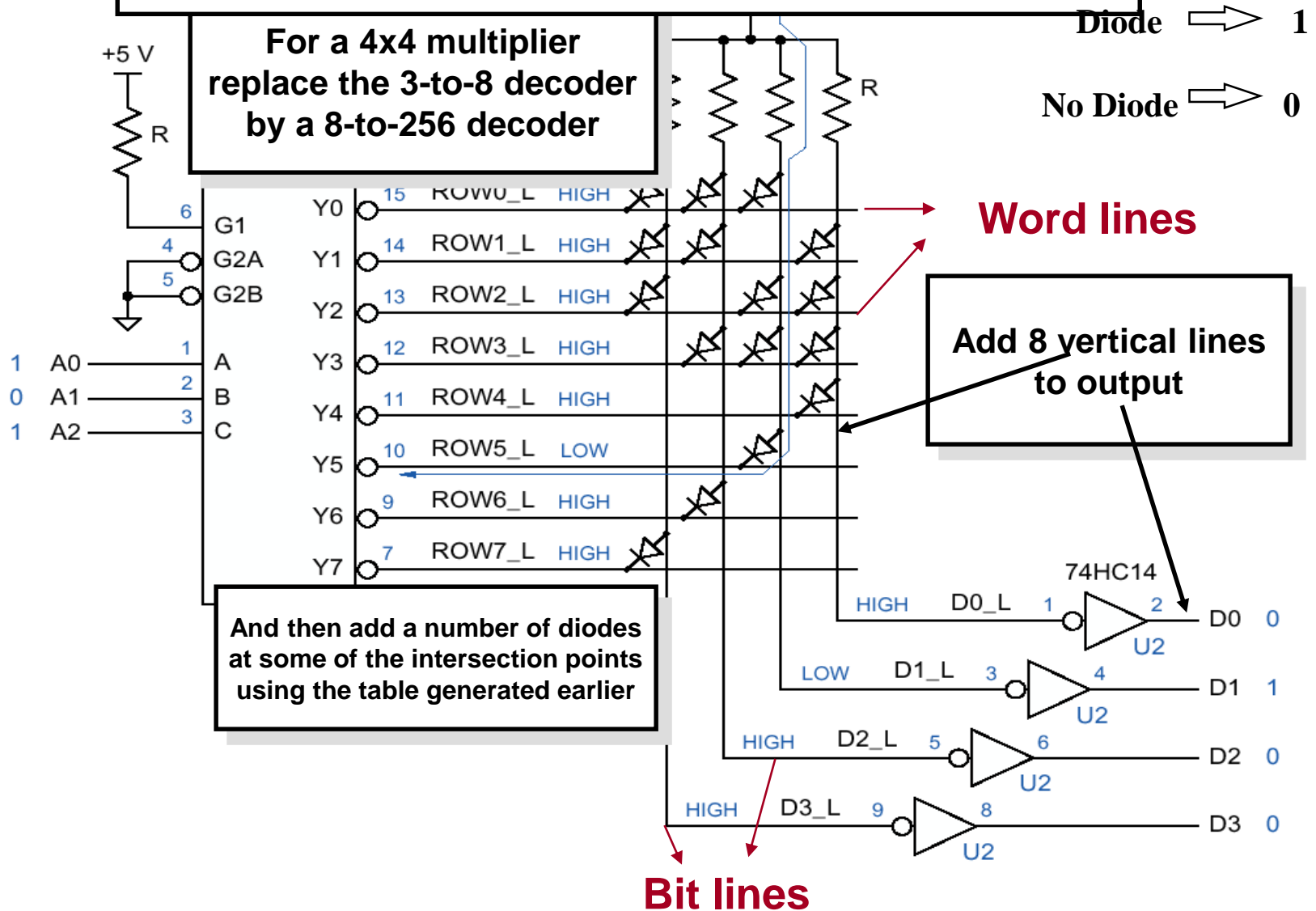
And you have a 4x4 multiplier that will be real fast






Two-dimensional decoding

128x1 ROM

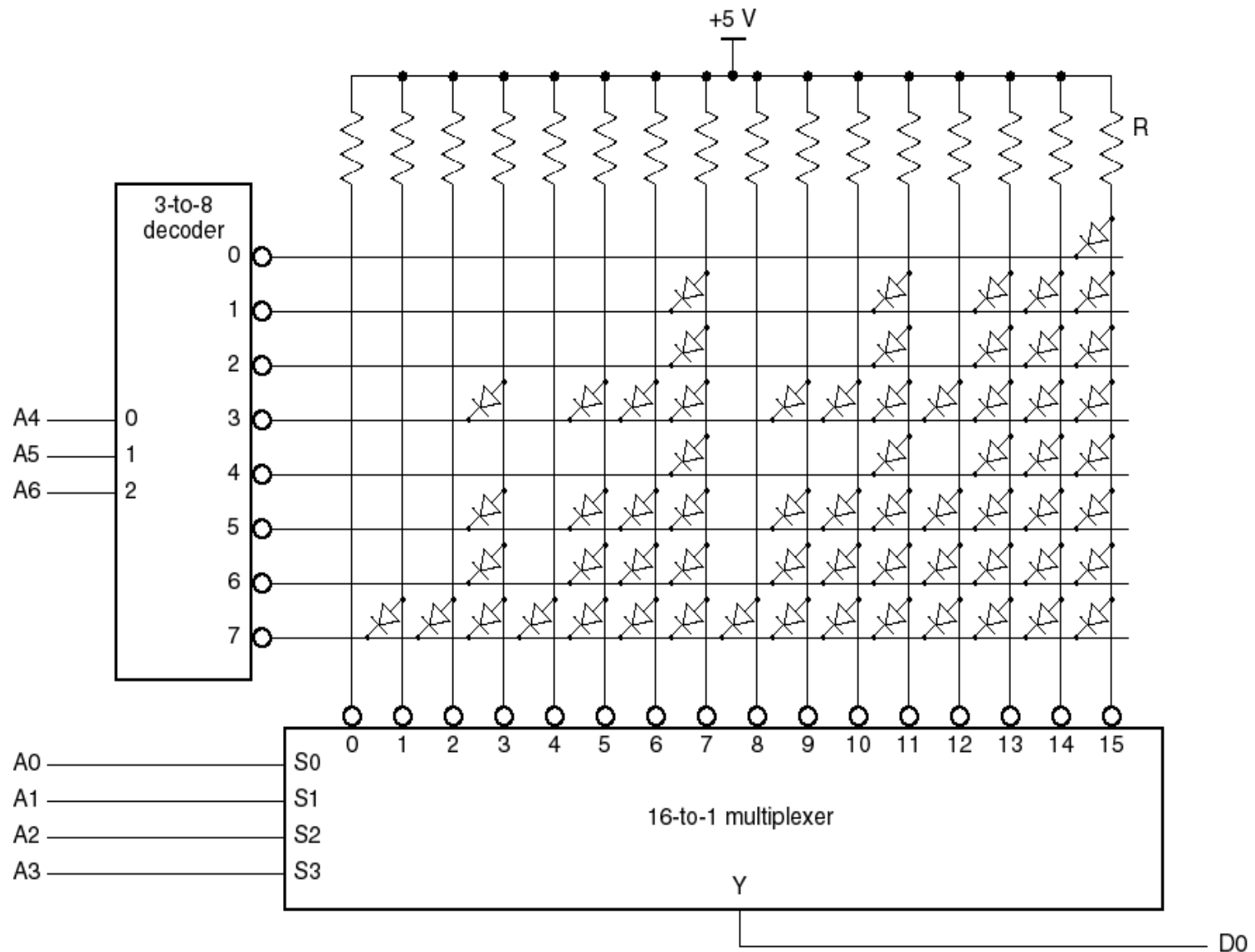




Larger example, 32Kx8 ROM

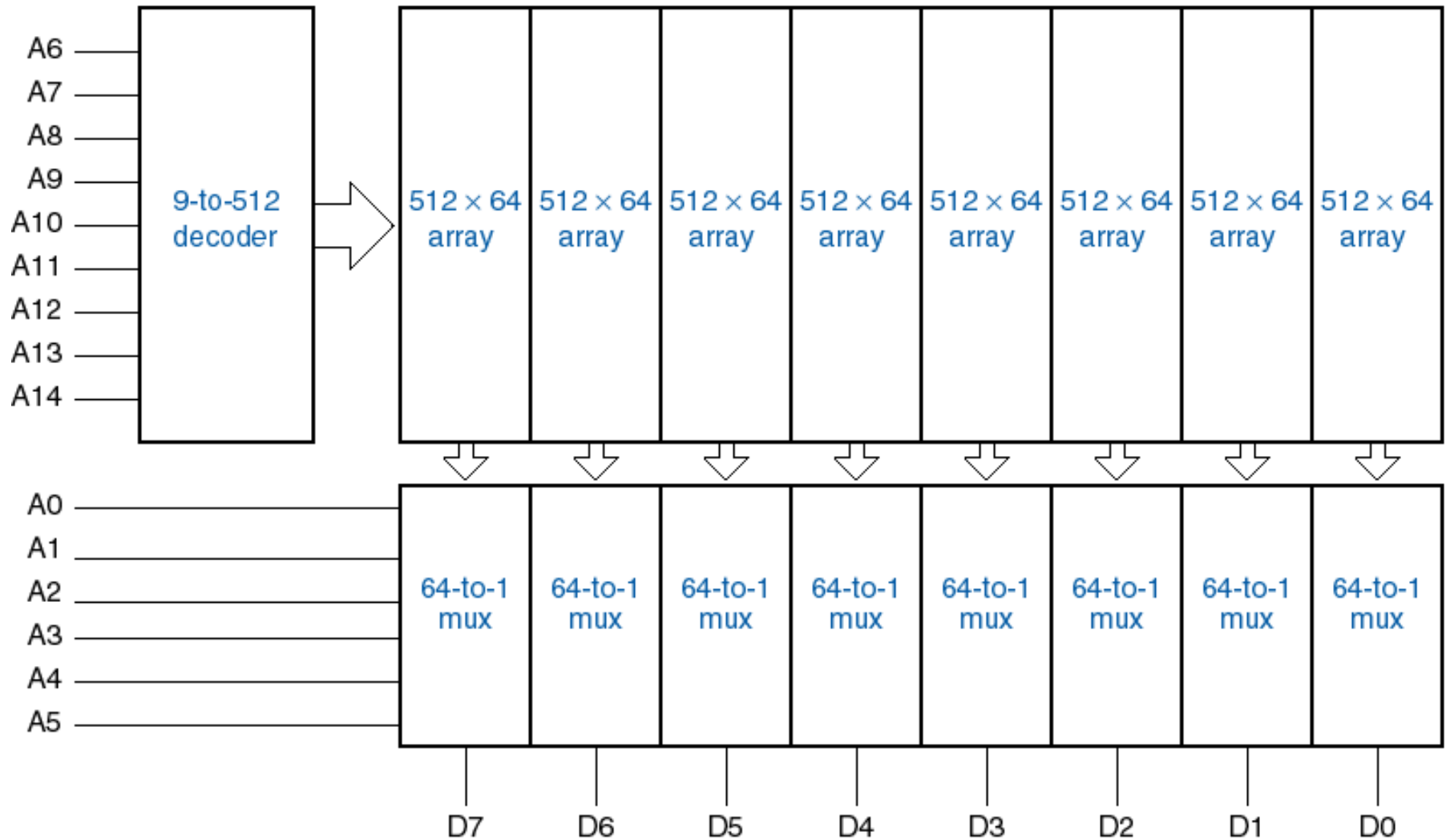



MOS Transistors as Storage elements

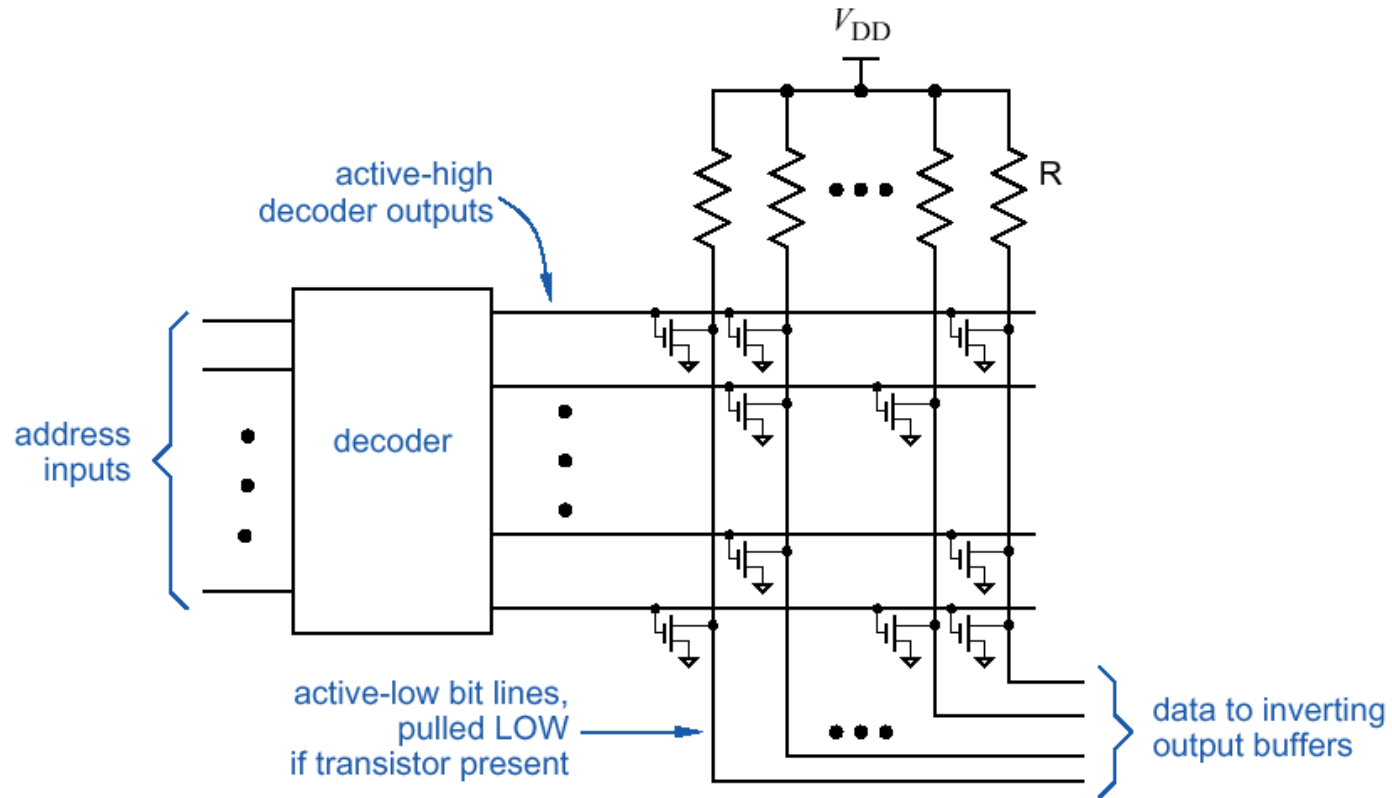

Transistor \Rightarrow 1

No transistor \Rightarrow 0



Using ROMs for Combinational Logic

☀ Two views of ROM:

- ☀ stores 2^n words of b bits each, or
- ☀ stores an n -input, b -output truth table

Example:


$n = 2$		$b = 4$			
A1	A0	D3	D2	D1	D0
0	0	0	1	0	1
0	1	1	1	1	1
1	0	0	0	0	1
1	1	1	0	0	0



Stores 4 4-bit words, or
stores 4 functions of 2
input variables



Diode ROM simplified diagram

 

Address decode: **AND** array:

$$W_0 = \bar{A}_1 \bar{A}_0$$

$$W_1 = \bar{A}_1 A_0$$

$$W_2 = A_1 \bar{A}_0$$

$$W_3 = A_1 A_0$$

Store: **OR** array:

$$D_0 = W_0 + W_1 = \bar{A}_1 A_0 + \bar{A}_1 \bar{A}_0$$

$$D_1 = W_3 + W_1 = A_1 A_0 + \bar{A}_1 A_0$$

$$D_2 = W_3 + W_2 + W_0$$
$$= A_1 A_0 + A_1 \bar{A}_0 + \bar{A}_1 \cdot \bar{A}_0$$


$$D_3 = W_3 + W_1 = A_1 A_0 + \bar{A}_1 A_0$$



 Example 1: using ROM to complete the function:

$$F_1(A, B, C, D) = m_1 + m_2 + m_6 + m_{10} + m_{11} + m_{12} + m_{13} + m_{14} + m_{15}$$

$$F_2(A, B, C, D) = m_0 + m_1 + m_3 + m_7 + m_8 + m_9 + m_{10} + m_{11} + m_{12} + m_{13} + m_{14} + m_{15}$$



ROM store capacity: $4 \times 14 \times 2$

注：容量 = 输入数 \times 乘积项数 \times 输出数



Example 2: using ROM to complete the conversion from binary code to gray code, draw ROM diagram.

B3 B2 B1 B0	G3 G2 G1 G0
0 0 0 0	0 0 0 0
0 0 0 1	0 0 0 1
0 0 1 0	0 0 1 1
0 0 1 1	0 0 1 0
0 1 0 0	0 1 1 0
0 1 0 1	0 1 1 1
0 1 1 0	0 1 0 1
0 1 1 1	0 1 0 0
1 0 0 0	1 1 0 0
1 0 0 1	1 1 0 1
1 0 1 0	1 1 1 1
1 0 1 1	1 1 1 0
1 1 0 0	1 0 1 0
1 1 0 1	1 0 1 1
1 1 1 0	1 0 0 1
1 1 1 1	1 0 0 0

choose $2^4 \times 4$ ROM

input : B_3 、 B_2 、 B_1 、 B_0 , address 4-bit;

output: G_3 、 G_2 、 G_1 、 G_0 , data 4-bit;


 B_0 B_1 B_2 B_3 W_0 W_1 W_2 W_3 W_4 W_5 W_6 W_7 W_8 W_9 W_{10} W_{11} W_{12} W_{13} W_{14} W_{15} G_0 G_1 G_2 G_3



Typical commercial EEPROMs


8K × 8

2764

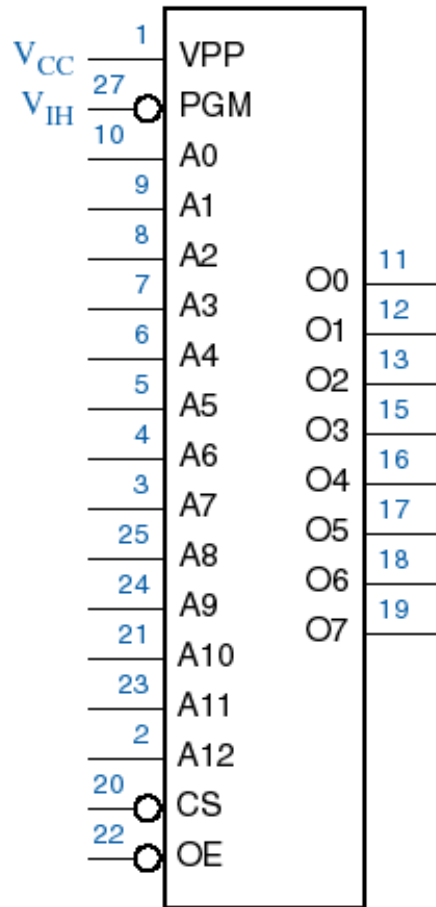


16K × 8

27128

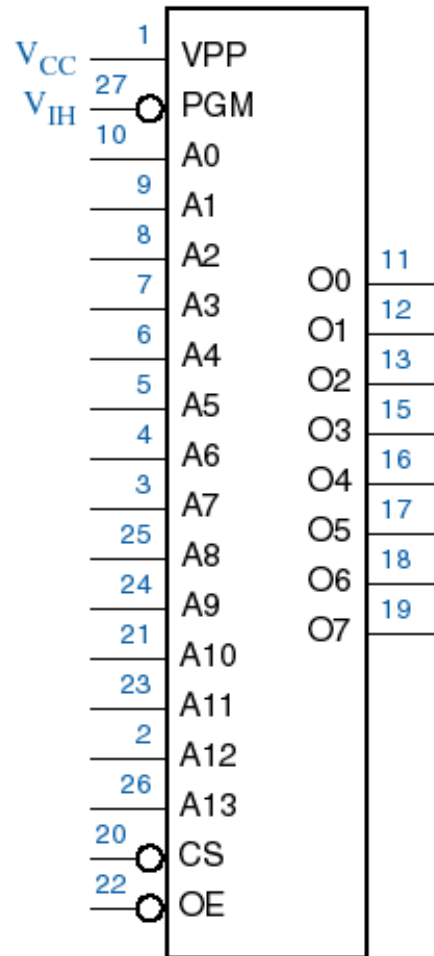


32K × 8

27256

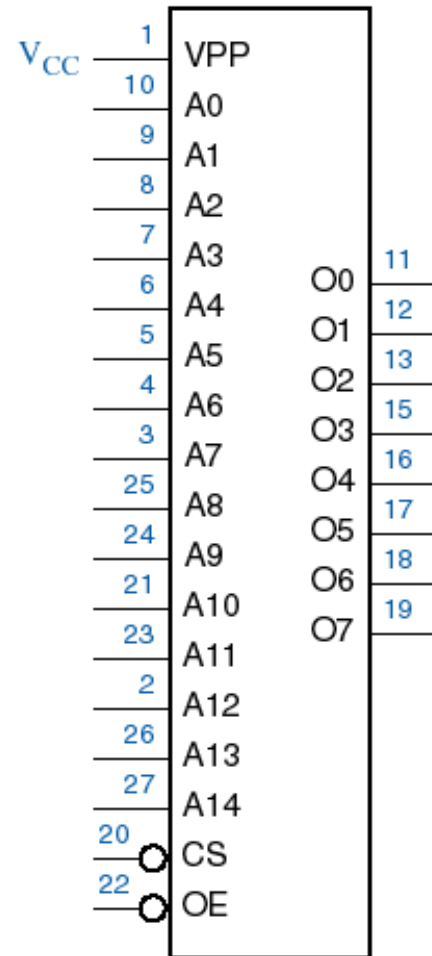


64K × 8

27512

 




Microprocessor EPROM application

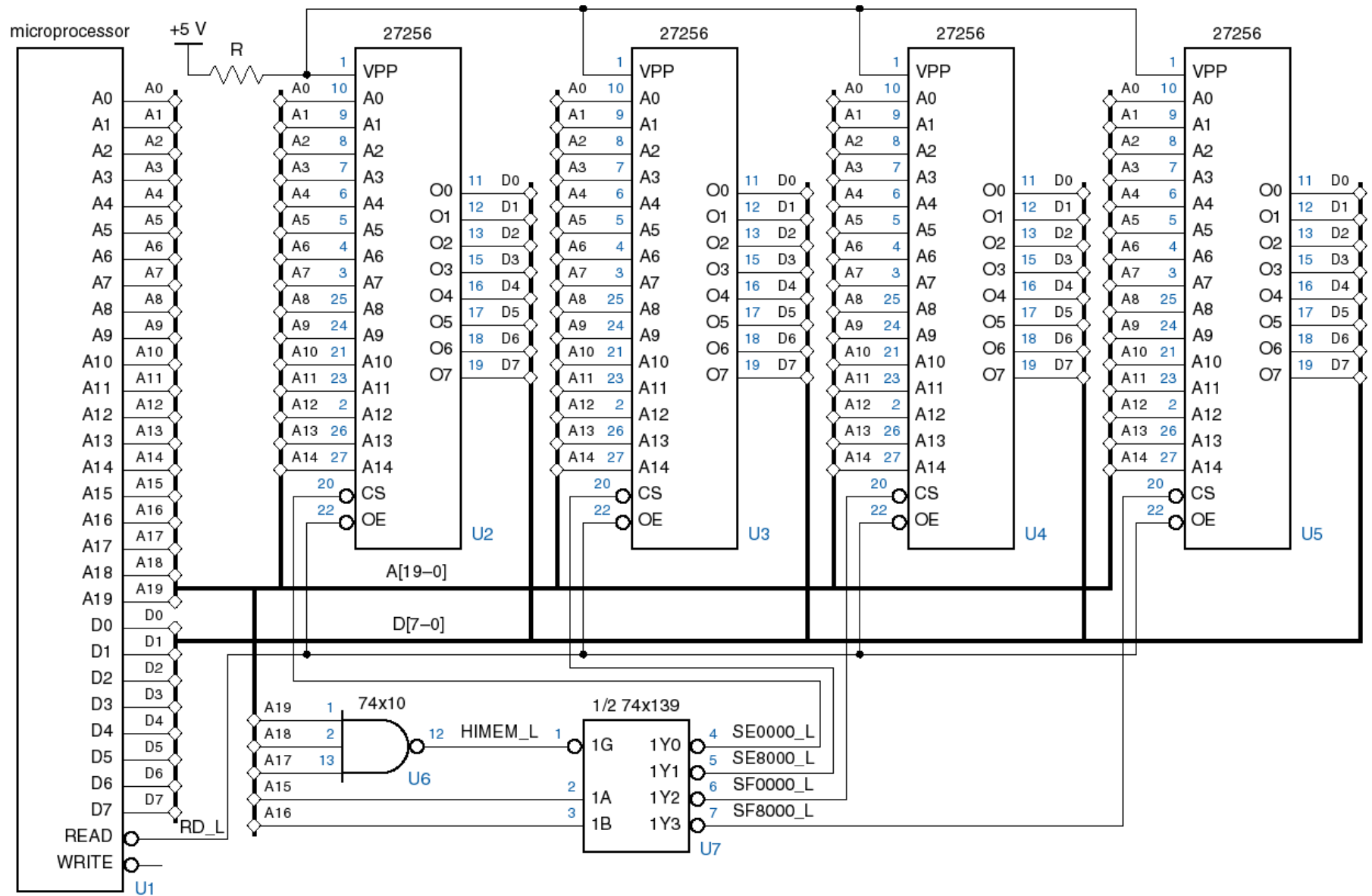




ROM control and I/O signals

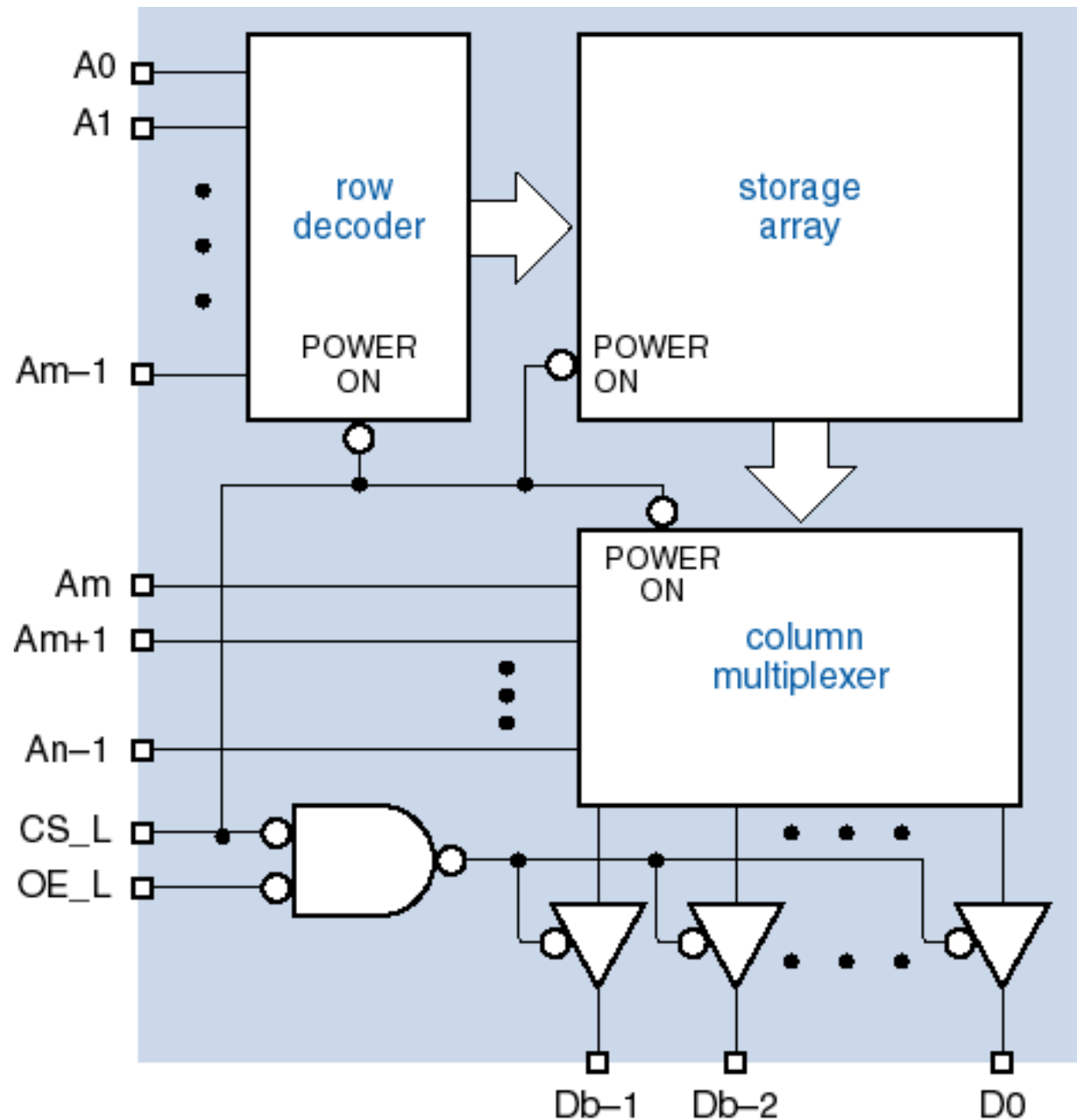



ROM timing

 

输出禁止时段




Read/Write Memories

- ✦ a.k.a. “RAM” (Random Access Memory)
- ✦ Volatility
 - ✦ Most RAMs lose their memory when power is removed
 - ✦ NVRAM = RAM + battery
 - ✦ Or use EEPROM
- ✦ SRAM (Static RAM)
 - ✦ Memory behaves like latches or flip-flops
- ✦ DRAM (Dynamic Memory)
 - ✦ Memory lasts only for a few milliseconds
 - ✦ Must “refresh” locations by reading or writing



SRAM

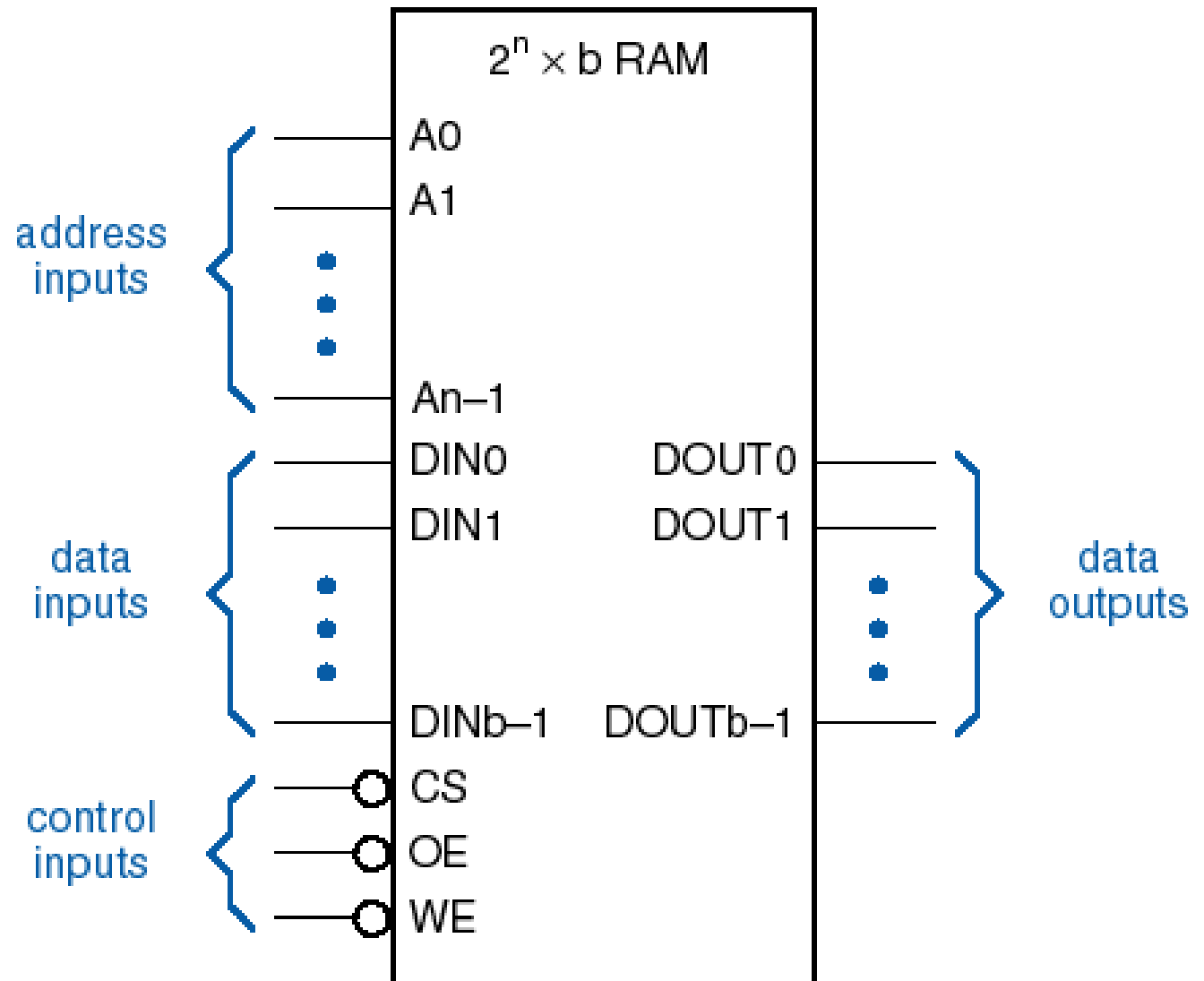


- ☀ Address/Control/Data Out lines (Reading)
- ☀ + Write Enable (WE) and Data In (DIN) (Writing)




SRAM operation

 - ☀ Individual bits are D latches, *not* edge-triggered D flip-flops.
 - ✳ Fewer transistors per cell.
- ☀ Implications for write operations:
 - ✳ Address must be stable before writing cell.
 - ✳ Data must be stable before ending a write.






SRAM array

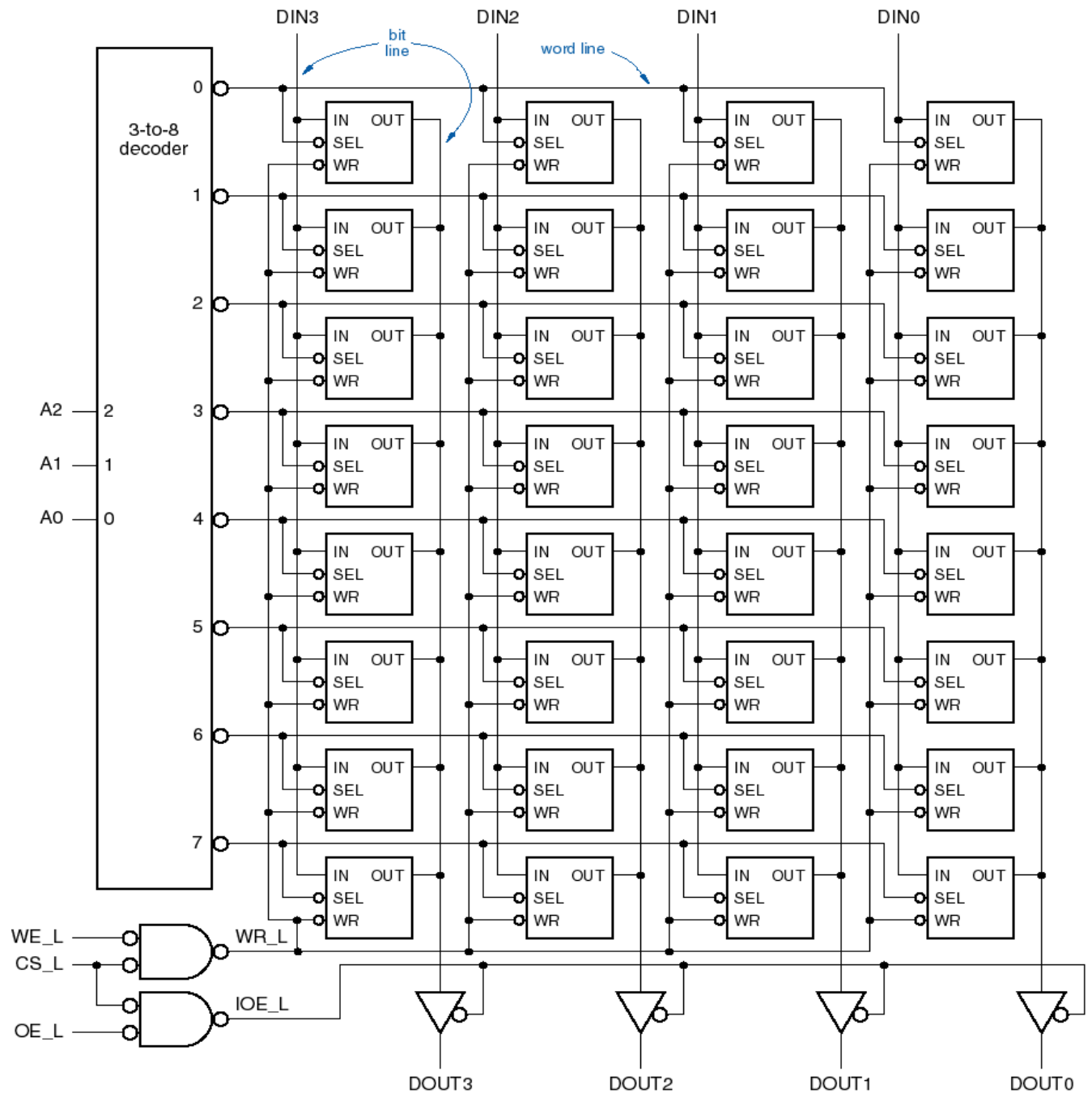



SRAM control lines

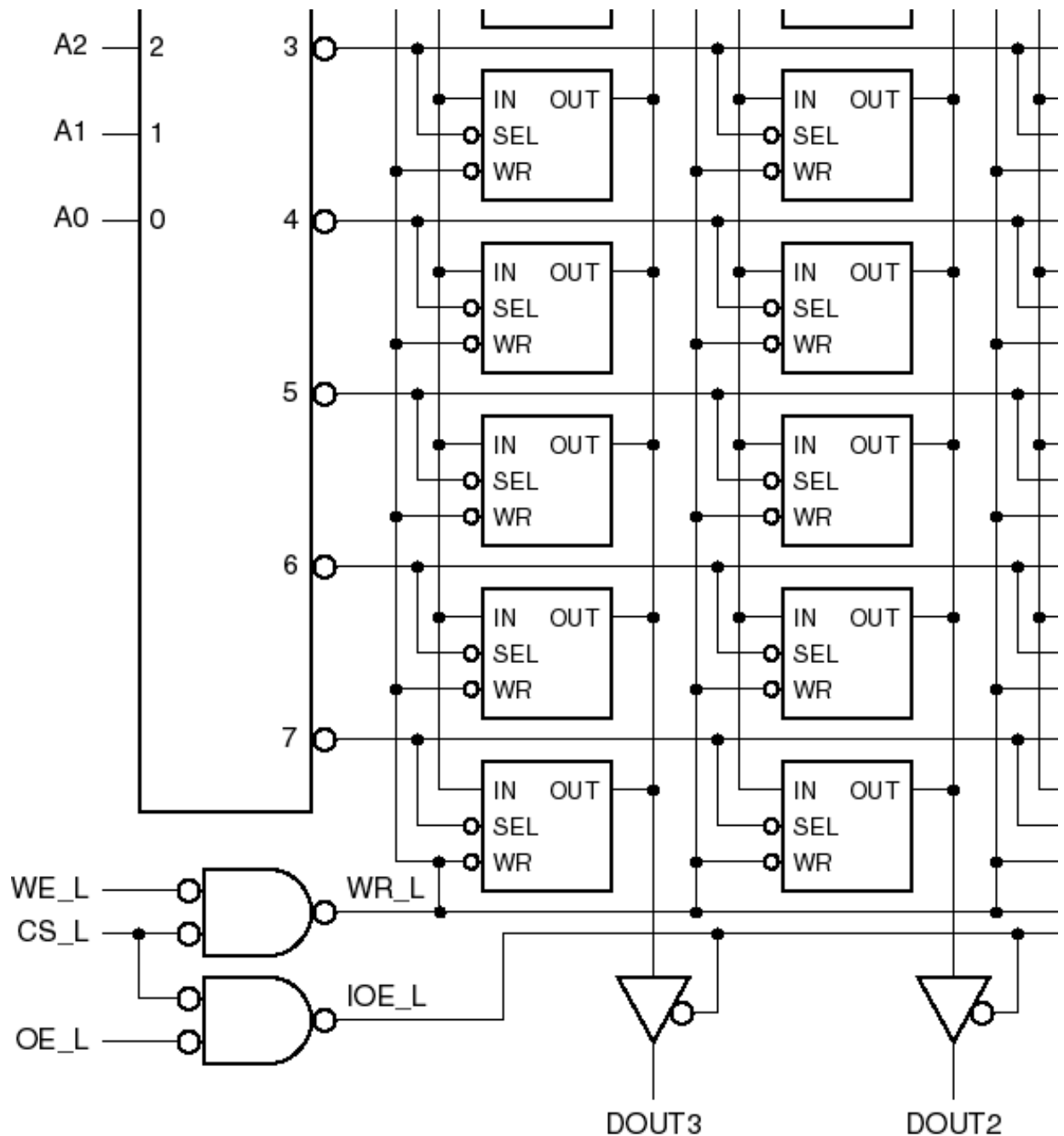
- ☀ Chip select
- ☀ Output enable
- ☀ Write enable






SRAM read timing

☀ Similar to ROM read timing

 




SRAM write timing

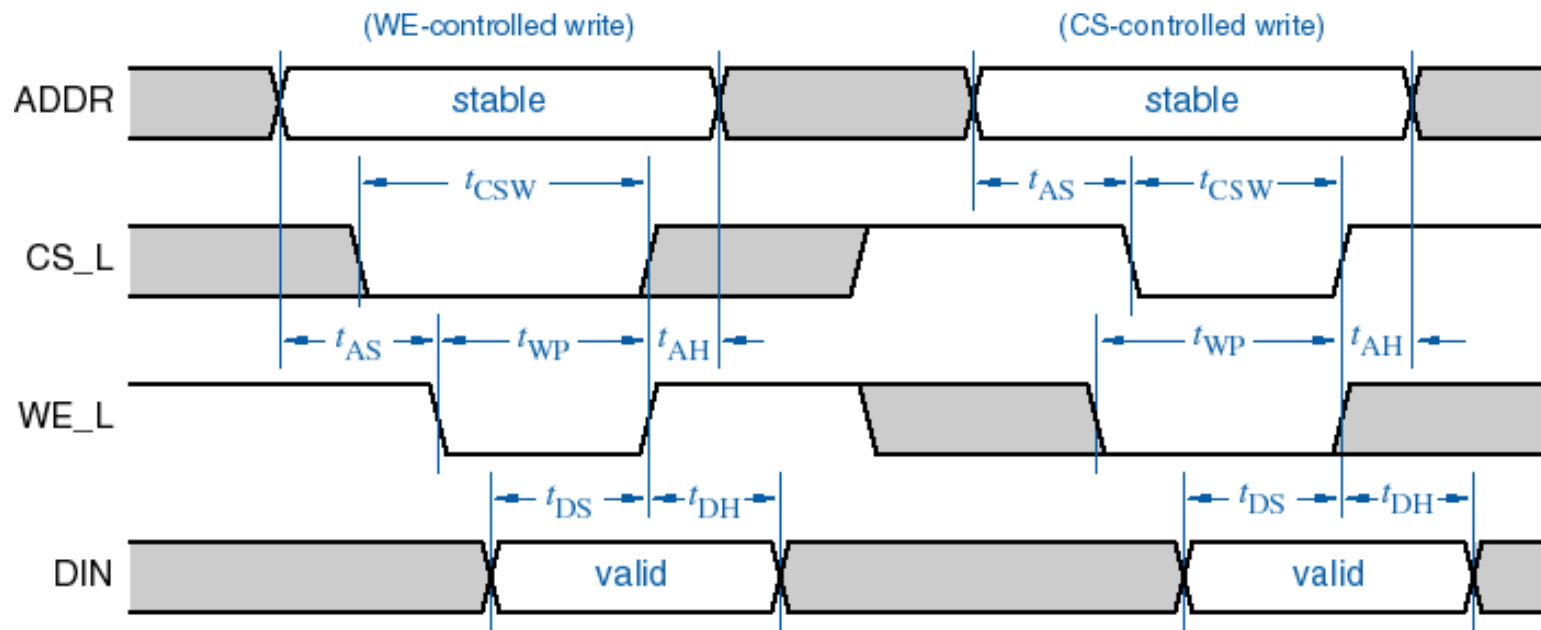

- ☀ Address must be stable before and after write-enable is asserted.
- ☀ Data is latched on trailing edge of (WE & CS).



Bidirectional data in and out pins




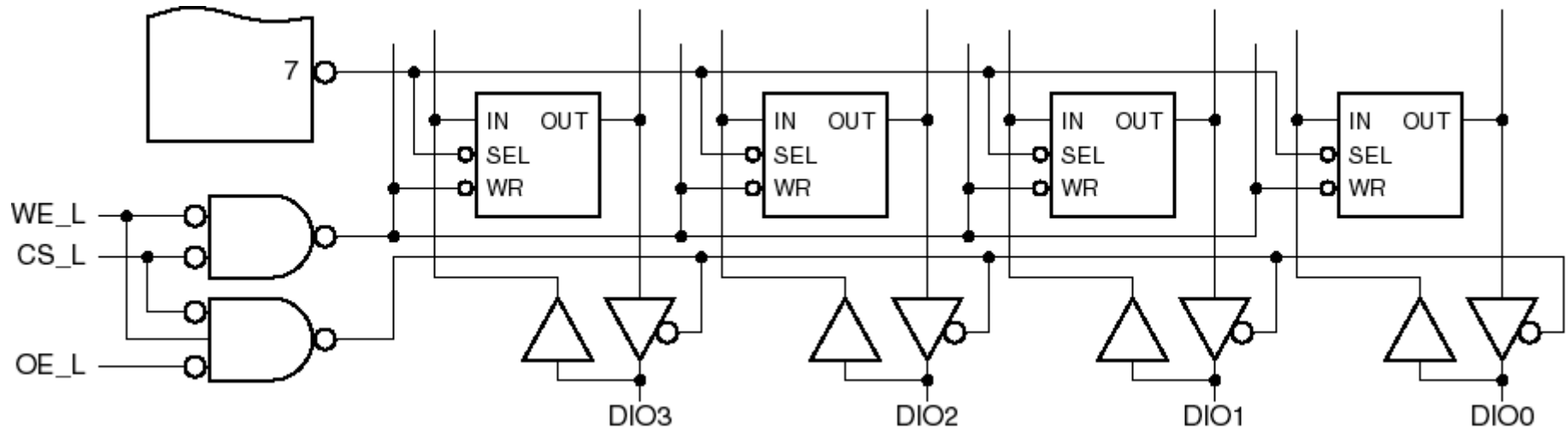


- ☀ Use the same data pins for reads and writes
 - ✳ Especially common on wide devices
 - ✳ Makes sense when used with microprocessor buses (also bidirectional)



SRAM devices


☀ Similar to ROM packages

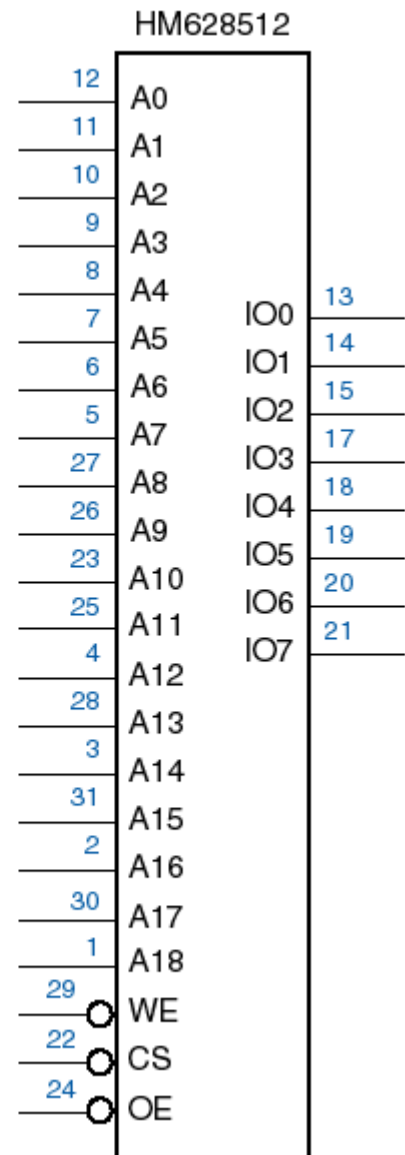  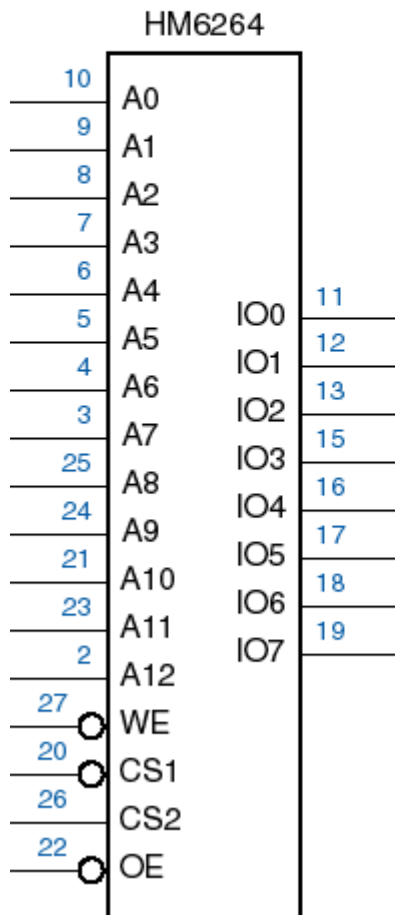



Expanding memory devices

 Examp.1: expand $64\text{K} \times 1$ RAM into $64\text{K} \times 8$ RAM




bit expanding :need 8 RAM chips

位扩展时，模块中所有芯片的地址线和控制线互连形成整个模块的地址线和控制线，而各芯片的数据线并列形成整个模块的数据线。



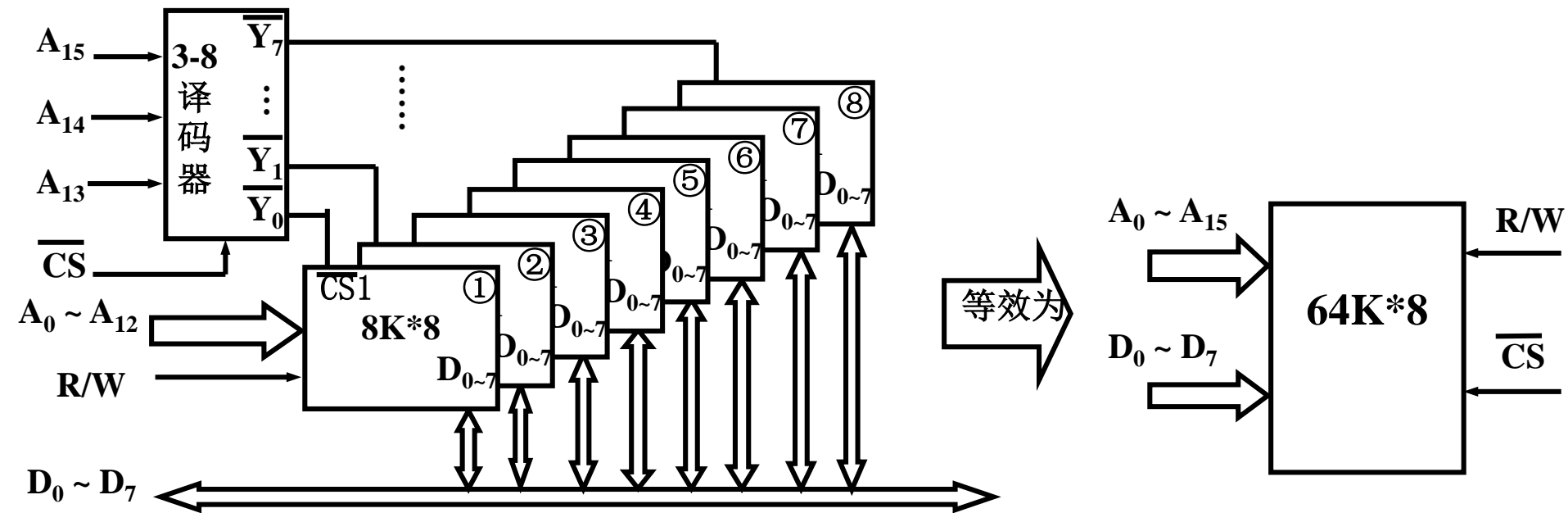Examp.2: expand $8K \times 8$ RAM into $64K \times 8$ RAM



word expanding: need 8 RAM chips

字扩展时，模块中所有芯片的地址线和读写信号线互连，扩展用的地址线可用来译码以形成对各个芯片的选择线（称为片选线）。

注：片选线的设计方法将确定每个芯片的地址范围。



1. A $4k \times 8$ ROM has () bits of storage, () address bits, and () output data bits.
2. The capacity of a 4MB SRAM is expanded to () if there is a 2-bit increase in its address.
3. To implement a logic circuit with 4 inputs and 3 outputs using a ROM, a () ROM is required, at the very least.

解析：考查要点，ch9存储器的内容。

1. 32k; 4k; 8; 2. $2^2 \times 4\text{MB} = 16\text{MB}$; 3. $2^4 \times 3$



4. A 1GB DRAM has ()address lines.

5. A 4×4 unsigned binary multiplication can be built with a () ROM.

A. 128×4 B. 256×4

C. 128×16 D. 256×8

参考答案:

4. 30;

5. D 解析: 4×4 乘法运算, 寻址线为8根, 寻址能力为 $2^8=256$, 而数据线也为8根, 故选D